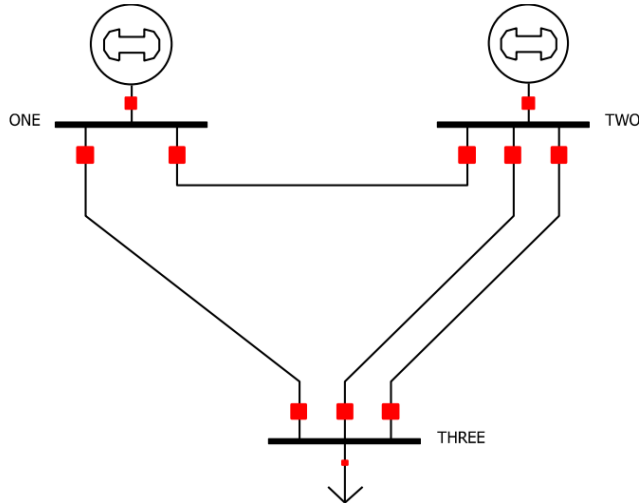


Gauss-Seidel example (Base power is $S_B=100$ MVA):



Bus	Voltage (p.u.)	Power
1	1.02	(slack)
2	1.02	$P_G=50$ MW
3	-	$P_C=100$ MW $Q_C=60$ MVar

Lin	Impedance (p.u.)
1-2	$0.02+0.04j$
1-3	$0.02+0.06j$
2-3	$0.02+0.04j$ (each)

Solution procedure:

1. Data and unknown:

Bus	Type	Data	Unknown
1	Slack	$V_1=1.02$ $\delta_1=0.0$	P_1 Q_1
2	PV	$V_2=1.02$ $P_2=0.5$	δ_2 Q_2
3	PQ	$P_3=-1.0$ $Q_3=-0.6$	δ_3 V_3

2. Y_{BUS} calculation:

$$Y_{BUS} = \begin{bmatrix} 15-35j & -10+20j & -5+15j \\ -10+20j & 30-60j & -20+40j \\ -5+15j & -20+40j & 25-55j \end{bmatrix}$$

3. Voltage magnitude initialization (iteration 0):

$$V_3 = V_3^0 = 1 \quad \text{PQ bus}$$

$$\left. \begin{array}{l} \delta_2 = \delta_2^0 = 0 \\ \delta_3 = \delta_3^0 = 0 \end{array} \right\} \text{All buses but the reference one}$$

Vector form:

$$V^0 = \begin{bmatrix} 1.02 \\ 1.02 \\ 1 \end{bmatrix} \quad \delta^0 = \begin{bmatrix} 0 \\ 0 \\ 0 \end{bmatrix}$$

Per iteration:

- PV buses (Q, δ) $i=2, \dots, m$ (bus 2)

- PQ buses (V, δ) $i=m+1, \dots, n$ (bus 3)

- Stopping criterios:

a) convergence $\rightarrow S_{slack}$ and power flows;

b) no converge \rightarrow new iteration

4. PV buses: iteration (r+1) :

\rightarrow bus 2:

$$Q_2^{(r+1)} = -\Im \left\{ (\bar{V}_2^{(r)})^* \bar{Y}_{21} \bar{V}_1^{(r+1)} + (\bar{V}_2^{(r)})^* \bar{Y}_{22} \bar{V}_2^{(r)} + (\bar{V}_2^{(r)})^* \bar{Y}_{23} \bar{V}_3^{(r)} \right\}$$

$$\delta_2 = \text{angle}[\bar{V}_2] \quad \bar{A}_2^{(r+1)} = \frac{P_2 - jQ_2^{(r+1)}}{\bar{Y}_{22}}$$

$$\delta_2^{(r+1)} = \text{angle} \left\{ \frac{\bar{A}_2^{(r+1)}}{(\bar{V}_2^{(r+1)})^*} - \bar{B}_{21} \bar{V}_1^{(r+1)} - \bar{B}_{23} \bar{V}_3^{(r)} \right\}$$

where

$$\bar{B}_{ik} = \frac{\bar{Y}_{ik}}{\bar{Y}_{ii}} \text{ is a constant}$$

5. Buses PQ iteration (r+1):

→ bus 3:

$$\bar{V}_3^{(r+1)} = \frac{\bar{A}_3}{(\bar{V}_3^{(r)})^*} - \bar{B}_{31} \bar{V}_1^{(r+1)} - \bar{B}_{32} \bar{V}_2^{(r+1)}$$

where

$$\left. \begin{aligned} \bar{A}_3 &= \frac{P_3 - jQ_3}{\bar{Y}_{33}} \\ \bar{B}_{ik} &= \frac{\bar{Y}_{ik}}{\bar{Y}_{ii}} \end{aligned} \right\} \text{ Are constants for PQ buses}$$

6. Stopping criterion:

$$\varepsilon = 10^{-3}$$

$$\left. \begin{aligned} |V_i^{(r+1)} - V_i^{(r)}| \\ \& \\ |Q_j^{(r+1)} - Q_j^{(r)}| \end{aligned} \right\} < \varepsilon \quad i = 2, 3; j = 2$$

If convergence:

6.1) Slack power:

$$\bar{S}_{\text{slack}}^* = P_1 - jQ_1 = \bar{V}_1^* (\bar{Y}_{11} \bar{V}_1 + \bar{Y}_{12} \bar{V}_2 + \bar{Y}_{13} \bar{V}_3)$$

6.2) Power flows:

$$\bar{S}_{12}, \bar{S}_{21}, \bar{S}_{13}, \bar{S}_{23}, \bar{S}_{31}, \bar{S}_{32}$$

$$\bar{S}_{ik} = \bar{V}_i (\bar{V}_i^* - \bar{V}_k^*) \bar{Y}_{Lik}^*$$

6.3) Line losses:

$$\bar{S}_{\text{loss},ik} = \bar{S}_{ik} + \bar{S}_{ki} \quad k,i = 1,2,3$$

$$\bar{S}_{\text{loss}} = \bar{S}_{\text{loss},12} + \bar{S}_{\text{loss},13} + \bar{S}_{\text{loss},23}$$

7. If no convergence, the procedure continues in Step 4.

Solution:

11 iterations needed to attain the solution:

Iteration (pu)	1	2	3	...	10	11
$P_1, Q_1(\text{slack})$	-	-	-	...	-	0.5083 0.0716
P_2	0.5	0.5	0.5	...	0.5	0.5
Q_2	0.81	0.4084	0.4696	...	0.5493	0.5501
P_3	-1.0	-1.0	-1.0	...	-1.0	-1.0
Q_3	-0.6	-0.6	-0.6	...	-0.6	-0.6

Iteration	1	2	3	...	10	11
V_1	1.02	1.02	1.02	...	1.02	1.02
$\delta_1(^{\circ})$	0	0	0	...	0	0
V_2	1.02	1.02	1.02	...	1.02	1.02
$\delta_2(^{\circ})$	0.0675	-0.1596	-0.2885	...	-0.4667	-0.4685
V_3	1.0041	1.0042	1.0043	...	1.0043	1.0043
$\delta_3(^{\circ})$	-0.5746	-0.7336	-0.8278	...	-0.9580	-0.9593

Final Solution:

Bus	P (MW)	Q (MVar)	\bar{V} (pu)
1	50.83	7.16	1.02 $\angle 0^{\circ}$
2	50.00	55.01	1.02 $\angle -0.4685^{\circ}$
3	-100	-60.00	1.0043 $\angle -0.9593^{\circ}$